

Pheostat, variac  
No: ↓ P ↓ V

Date: / /

- KCL - algebraic sum of currents at a junction is zero
  - KVL - algebraic sum of all voltages around a closed loop is zero.
- G gen.      active       $\rightarrow$  ideal       $\rightarrow$  non-ideal      (voltage source)
- passive      linear RLC      generators      I " "
- $\rightarrow$  non-linear diode, transistors
- I flows  $\rightarrow$  unidirectional PN diode  
bidirectional R, CL

hydro

Victoria  
(Asha Pana)  
Kotmale

low maintenance cost

' fuel cost (free) water

disadv

capital cost ↑

vulnerable to adverse weather conditions

fuel (coal, oil)  
(thermal)

can be

situated near source  
reducing fuel transmission  
cost

env. pollution

fuel cost ↑

steam turbine

gas

norochcholi, kerawalapitiya

high efficiency

risk of radiation leaks

nuclear

waste disposal (management)

waste is harmful to env & human

wind

puttalam rural electrification  
Hambantota

not consistent (continuously available)


Solar

"

high capital cost

low efficiency (20-30%)

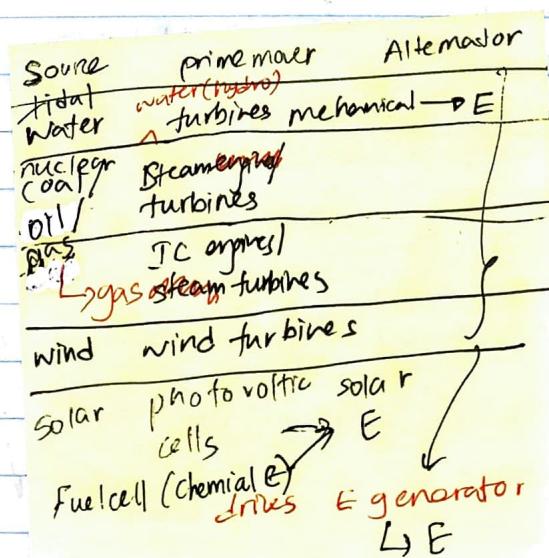power consumption  
power loss (heat)  
no hum, flickery



OTEC

ocean thermal E

conv

+  
comp.  
gas

Trincomalee  
minewater

gas  
turbine

coherent unit system  $\rightarrow$  sys of units used to measure physical qts.  
 sys units that are defined s.t. eg<sup>u</sup> relating numerical values  
 defined using base expressed in units of sys. have exactly same form  
 same form, numerical factors including numerical factors, as the corresponding eg<sup>u</sup> directly  
 relating qts.


- resistivity vs resistance  $\rightarrow$  peak factor =  $\frac{\text{peak}}{\text{rms}} = \sqrt{2}$
- conductivity vs conductance

$$\text{Form factor} = \frac{\text{rms}}{\text{avg}}$$

- Admittance  $\rightarrow S$  ( $a, B, R, x$  all +ve)

- angular frequency ( $\omega$ ) vs frequency (Hz)

phasor diagram

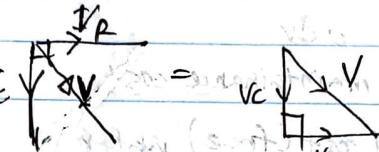

$$S = r\theta$$

$$A = r^2 \theta_{\text{sr}}$$

- CEB 33 kV, ECO 11 kV } 2  $\mu$ F

$$B \Omega \quad 8\Omega \quad 10\Omega$$

$$5 + j(+8 - 10) = 5 + j 2 \Omega_{\parallel}$$

$$\nabla^2 V = -\rho \quad \text{charge density}$$

+ Poisson's

$$\epsilon \nabla^2 V = 0 \quad \text{permittivity}$$

$\rho = 0$  Laplace  $\rightarrow$   $V$  potential field is zero in a source-free region

abs. permittivity of dielectric mat (F/m)

$$C = \frac{\epsilon A}{d} \quad \text{surface Area} \quad \text{conductive media} \quad Q = CV$$

$d$  distance between plates

$$L = \frac{\phi_B}{I} = \frac{N^2 A M_0}{l} \quad \text{Number of turns in wire coil}$$

$$V = IR$$

$$V = L \frac{di}{dt} \rightarrow L = \frac{\phi}{I}$$

$$I = kA$$

$$\phi = kI$$

$$I = n A v Q \quad \text{length of coil}$$

$$\# \text{ electrons} \quad \text{Surface Area} \quad \text{drift velocity}$$

charge density  $(\text{m}^{-3})$  cross section (cross sectional area)

resistivity  $(\Omega m)$

$$R = \rho \frac{l}{A} \quad \text{length of conductor}$$

$$A = \text{surface Area of conductor. (cross sectional Area)}$$

electricity  $\rightarrow$  type of E, occurs naturally / produced, expressed flow of e- charge current

AC theory

- Peak value = max + / -
- $f_{\text{harmonics}} = n \times f_{\text{fundamentals}}$
- odd/even periodic alternating  $\rightarrow$  magnitude ↑ alternating + / 0
- leads / lags  $\phi$
- $V_{\text{mean}} = \frac{\int V(t)}{T}$  area with +/- one cycle
- $V_{\text{avg}} = \frac{\int v(t)}{T/2}$  half (+) cycle or rectified full cycle
- $\sqrt{V_{\text{rms}}} = \sqrt{\frac{\int V^2(t)}{T}}$
- Sin usoid
  - $V_{\text{mean}} = 0$
  - $V_{\text{avg}} = \frac{2 V_m}{\pi}$
  - $\sqrt{V_{\text{rms}}} = \frac{V_m}{\sqrt{2}}$
  - peak = abs. max  $\omega = 2\pi f$   $T = \frac{1}{f}$  peak - peak val (abs distance)
- Form factor =  $\frac{\text{rms}}{\text{avg}}$
- Peak factor =  $\frac{\text{Peak}}{\text{rms}}$
- advantages of AC over DC production → economical & stepped up & down to DC

peak values radians in rad

$v(t) = V_m \cos(\omega t - \phi)$

$V = 10 \times 30^\circ$   $\sin(90 + (\omega t - \phi))$  (+)ve

$V \rightarrow 240V/50Hz$

- \* Units A, V, Ω, rad<sup>-1</sup>
- polar  $\rightarrow V_{\text{rms}} < \phi$  state whether lags/leads wrt. I or V
- cartesian  $\rightarrow V_{\text{rms}} (\cos \phi + j \sin \phi) = V_{\text{rms}} e^{j\phi}$

Impedance  $Z = \frac{V}{I} = R + j X$  (12)  $\uparrow$  resistance  $\uparrow$  reactance

Admittance  $Y = \frac{1}{Z} = \frac{I}{V} = G + j B$  (12')  $\uparrow$  conductance  $\uparrow$  susceptance { \$ (siemens) \$ }

Resistor  $V = IR$   $\Rightarrow \frac{V}{I} = R$

Inductor  $V = L \frac{di}{dt} \cos 90^\circ$

Capacitor  $Q = CV \Rightarrow i = C V$   $I = C \frac{dv}{dt}$

Series  $Z_{\text{eq}} = Z_1 + Z_2 + \dots$

parallel  $\frac{1}{Z_{\text{eq}}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots$

keep it MF

R-L series  $Z = R + j \omega L$

R-C series  $Z = R - j \frac{1}{\omega C}$

L-C series  $Z = \frac{1}{R} + j \left( \omega L - \frac{1}{\omega C} \right)$

R-LC series  $Z = R + j \left( \omega L - \frac{1}{\omega C} \right)$

RLC parallel  $\frac{1}{Z} = \frac{1}{R} + j \frac{1}{\omega C}$

R-C ||  $Y = \frac{1}{R} - j \omega C$

L-C ||  $Y = \frac{1}{R} + j \left( -\omega C + \frac{1}{\omega L} \right)$

Series resonance  $\omega L = \frac{1}{\omega C} \Rightarrow Z_{\text{min}} \rightarrow I_{\text{max}}$

Shunt resonance  $\omega C = \frac{1}{\omega L} \Rightarrow Z_{\text{max}} \rightarrow I_{\text{min}}$

Power factor ( $P.f = \cos\phi$ ) mention leading/lagging w.r.t V



$L/C \rightarrow$  reactance ( $X$ )  $\rightarrow$  reactive power

$(Q) \rightarrow$  var  
volt ampere reactive } no net work done  
force goes back & forth btw.

apparent power ( $S$ )  $\rightarrow VI \rightarrow \frac{VA}{volt amperes}$

active power (P)  $\rightarrow VI \cos\phi \rightarrow W$  (watt)



$$VI \sin\phi = Q \text{ (reactive)}$$

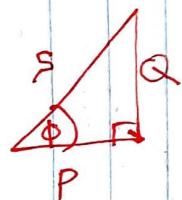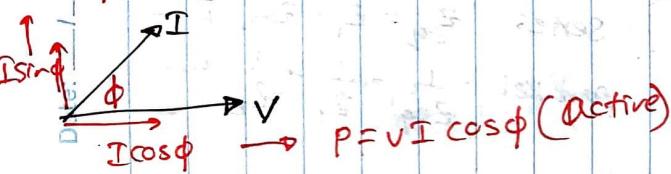

$$\text{power factor} = \cos\phi = \frac{P}{S}$$

leading power factor

lagging power factor

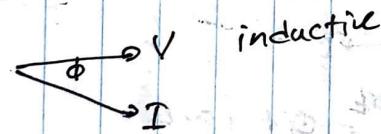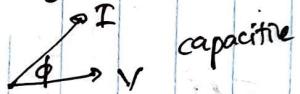

$$Y = 0.0154 - j0.0151$$

$$\text{for } p.f. \rightarrow 1 \quad \phi = 0 \rightarrow Y = \text{real}$$

$$\text{then susceptance needed} = +j0.0151$$


$$p.f. \downarrow \text{more current drawn from source} \quad |C\omega| = 0.0151$$

$\Rightarrow$  wire cost, power loss  $C = \checkmark$

capacitor parallel  
(pure reactance)

$$\text{capacitive reactance} = \frac{1}{j0.0151} = 66.2252 \Omega$$

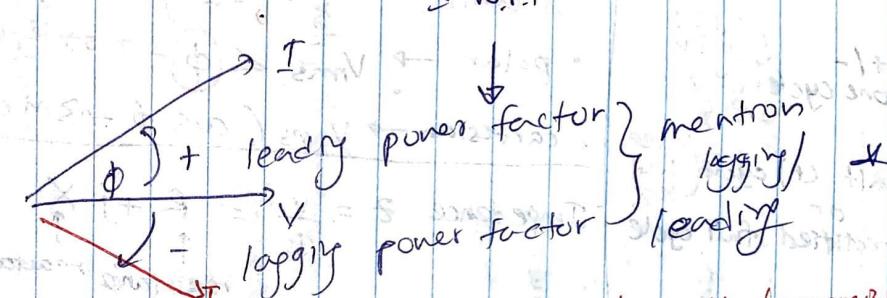more I reqd  
transfe same P  
with p.f.  $< 1$




high V transmission

$$P = IV \text{ LL}$$

$$\text{Loss} = I^2 R$$


economical

### 3-phase balanced system

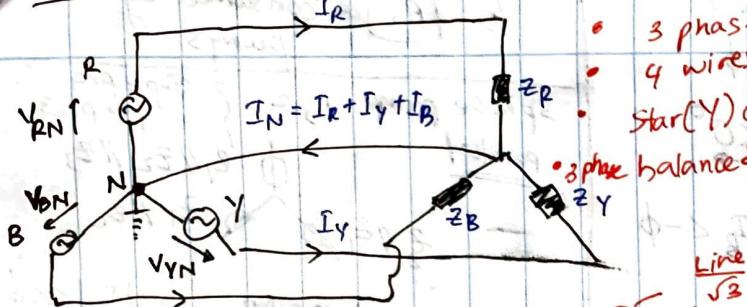

- 3 phase
- 4 wires (R Y B N)
- Star (Y) connected load
- 3 phase balanced source

phasor diagram balanced

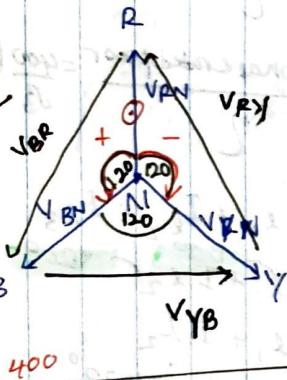

$$V_{RN} = E \angle 0^\circ$$

$$V_{YN} = E \angle -120^\circ$$

$$V_{BN} = E \angle +120^\circ$$

$$\text{KCL} \quad I_N = I_R + I_Y + I_B$$

$$= \frac{E \angle 0^\circ}{Z_P} + \dots$$

load balanced  $Z_P = Z_Y = Z_B = Z$   
 $\Rightarrow I_N = 0$  neutral wire is optional

$\boxed{\sqrt{3} |V_{\text{line-neutral}}|}$

RY  
RB  
YB  
Used line voltages

$V_L = \sqrt{3} V_{\text{phase}}$

e.g.: 400V, 50Hz, 22kW, 3-phase motor  
 line-line V rated output  
 mechanical power

- Why 3 phase needed over single phase?
- Why N needs to be earthed at the source?  
 ref! earth fault

### 3-phase balanced system

- line voltage  $\rightarrow$  phase voltage = phase current in Star (Y) connected loads
- line current  $I_E = 92 \text{ A}$  (no angles mentioned)
- $I_N = ? \quad 0 \Rightarrow \text{no power loss}$

• line resistance  $= I^2 R$

• line loss per phase  $= I^2 R$  if no current in N

• total line loss  $= 3 \times (I_{\text{line}}^2 R)$

• Power delivered by source per phase  $= |V| |I| \cos \theta$

• total power delivered by source  $= 3 |V| |I| \cos \theta$


• Power consumed by load per phase = power delivered by source per phase - line loss / power loss per phase

$|V_{\text{load}}| |I| \cos(\alpha)$

• total power consumed by load  $= 3 \times \text{power consumed by load per phase}$

• power transmission efficiency

per-phase equivalent circuit

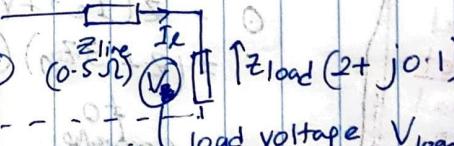

\* load voltage  $V_{\text{load}} = I \times Z$   
 phase  $\rightarrow$  convert to line voltage at the load

In balanced 3 phase  $\rightarrow$  N is optional in N wire

• total power delivered  $= 3 |V_L| |I_E| \cos \theta$

$= 3 |V_L| |I_E| \cos \theta$

$= \sqrt{3} |V_L| |I_E| \cos \theta$

3 phase active power  
 p.f. apparent  
 KVA  $\rightarrow \sqrt{3} |V_L| |I_E|$

power in balanced load/sys.


\* calculations done using phase voltages  
 \* answers given using line voltages

date:  
 non negligible even there's an impedance

take voltage as 0  
 In balanced 3-phase  
 N  $\rightarrow$  no current  
 no voltage  
 $\Rightarrow$  no power loss

total  $\rightarrow$  remember to multiply by 3  
 mention neutral wire loss

3 phase unbalanced

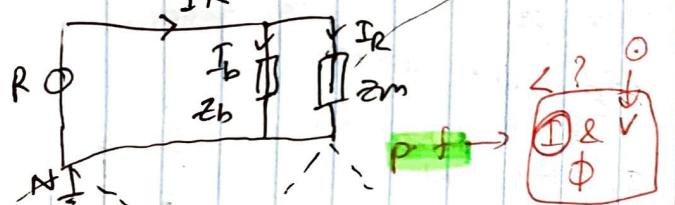

7kW, 230V, p.f 1.0 boiler  
boiler single phase load

$$P = |V| |I| \cos \phi$$

$$7 \times 10^3 = \frac{400}{\sqrt{3}} |I_b|$$

$$\text{then } I'_R = I_{R(\text{proj})} + I_b \\ = 134.72 \angle -41.41 + I_b \angle 0^\circ$$

$$\text{balanced power} = \sqrt{3} |V| |I| \cos \phi$$

$$I_N = I_{R(\text{proj})} + I_b + I_Y + I_B$$

$$= I_b \quad (\text{neutral wire will carry the return current})$$

$$\text{impedance (R)} \quad Z_b = \frac{400}{\sqrt{3}} \angle 0^\circ \quad I_b$$

$$Z_b / Z_m$$

Neutral is not optional now

show neutral wire B optional

$$\text{balanced} \rightarrow P = \sqrt{3} |V| |I| \cos \phi$$

$$I_R' = I_b \angle (-\phi) \quad V_R \angle 0^\circ$$

$$\text{then } I_Y = I_b \angle (-\phi - 120^\circ) \quad I_B \angle -\phi$$

$$I_B = I_b \angle (-\phi + 120^\circ)$$

$$\begin{aligned} \text{then KCL} \quad I_N &= I_R' + I_Y + I_B \\ &= 0 \quad \checkmark \end{aligned}$$

When neutral wire impedance cannot be neglected,  
Show sys is still balanced  
KVL to R loop  $I_N = I_R' + I_Y + I_B$

$$E \angle 0^\circ = I_R Z + I_N (Z_N)$$

+ 4, 5 loop


$$0 = Z(I_R + I_Y + I_B) + 3Z_N(I_R + I_Y + I_B)$$

$$= (Z + 3Z_N)(I_R + I_Y + I_B)$$

generally  $\neq 0$  still balanced

without N wire system unbalanced
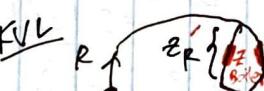
$$\text{KCL} \quad I_R' + I_Y + I_B = 0 \quad \text{--- (1)}$$



$$\frac{400}{\sqrt{3}} \angle 0^\circ - \frac{400}{\sqrt{3}} \angle +120^\circ =$$

$$I'_R Z_R - I_B Z_B \quad \text{--- (2)}$$



$$\frac{400}{\sqrt{3}} \angle 120^\circ - \frac{400}{\sqrt{3}} \angle -120^\circ =$$

$$Z_B I_B - Z_Y I_Y \quad \text{--- (3)}$$

$$\eta = \frac{P_o}{P_i} \text{ rated power (given) consumed by pumps}$$

3phase pump 1, 2 { single phase pump 3 parallel

$$Z_1 // Z_2 // Z_3$$

$$\text{power 3-phase pump} = \frac{400}{\sqrt{3}} |I_R'| \cos \phi$$

$$(3) \quad \eta$$

$$\text{single phasorated power} = \frac{400}{\sqrt{3}} |I_{l_3}| \cos \phi$$

$$I_R = I_{l_1} + I_{l_2} + I_{l_3}$$

$$I_Y = I_{l_1} + I_{l_2} \angle -120^\circ$$

$$I_B = I_{l_1} + I_{l_2} \angle +120^\circ \quad + 120^\circ \quad + 20^\circ$$

since 3-phase motors are balanced loads  $I_{l_i}$  = 1 phase current

$$= I_R + I_Y + I_B \quad \checkmark$$

find  $I'_R, I'_Y, I'_B$

phase voltages at the load

$$Z_R I'_R$$

$$Z_B I_B$$

$$Z_Y I_Y$$

motor currents are original current  $I_R = \frac{Z_R I'_R}{Z_m}$

Electrical installation ? combination of e. equip., specific purp., <sup>coordinated</sup> characteristics

1) why E equip./sys. needs to be protected?

2) From what do we need protection

3) protection methods (3)

4) What is earthing

5) protection for earth faults

CB → RCCB

6) protection for over currents / excess I

CB → MCB  
Fuses

7) fuses → current ratings

fusing current

fusing factor

8) types of fuses

re-wirable/semi enclosed

disadvantages

advantages

cartridge

\* HRC (high rupturing capacity)

9) MCB → types of mechanism and for what protection

10) adv. of MCB over fuses

11) types of earth leakage prot. type of operation remarks

ELCB

RCCB

\* 12) types of earthing regulations? → neutral equipment

13) types of earthing arrangements

TN N → direct electrical connection of the exposed conductive parts of consumer





TT first T, second T to supply earthed point (in AC → neutral)

IT I → isolated (All live parts are isolated from E / one point is connected to E through high Z)

14) Domestic installation → equip. belong to utility side / service provider consumer

15) Socket outlet wiring types

16) electric shock

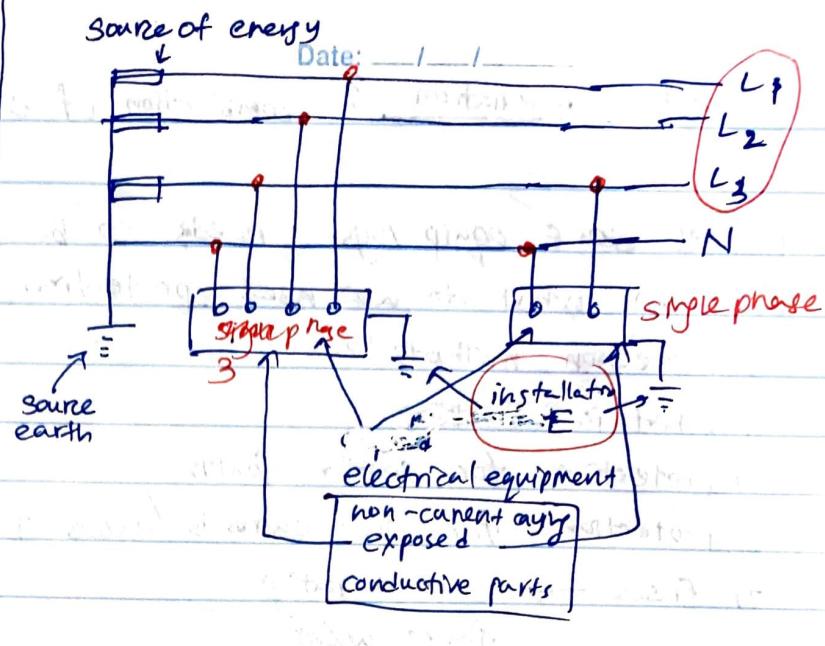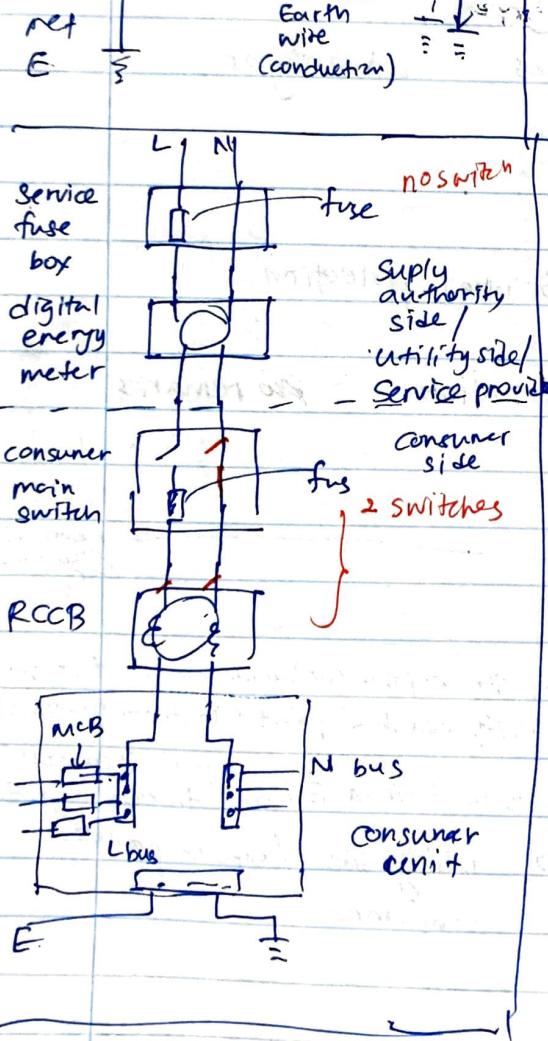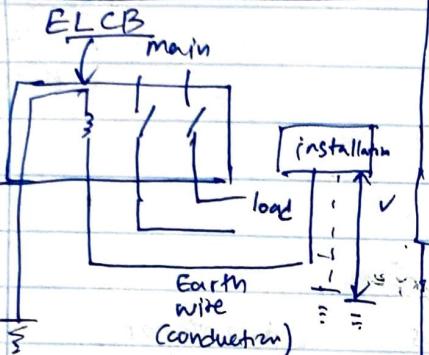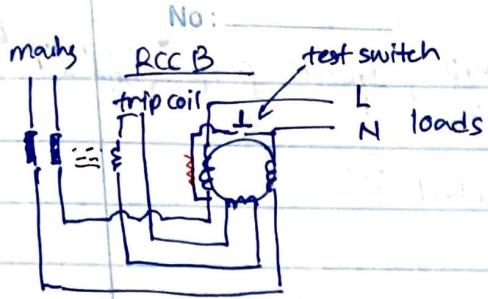

electrical installation tests,

- Continuity test L N G

- insulation test L ↔ L, L ↔ E

N has Z ~~if IN 70~~

V NFO